

Pratyush Saini

2019CS10444

## CO1215 Assignment 2.

- Overview of the design of digital clock.

### Modes of Digital Clock.

i) HH:MM

ii) MM:SS

where HH denotes the hours in decimal representation (0-23)  
MM denotes the minutes in decimal representation (0-59)  
SS denotes the seconds in decimal representation (0-59).

$$\begin{array}{c} H_1 H_2 : M_1 M_2 : S_1 S_2 \\ \underbrace{\hspace{1.5cm}}_{(i)} \quad \underbrace{\hspace{1.5cm}}_{(ii)} \end{array}$$

- Role of Push buttons

$b_0$  : Change the mode of clock from (i) to (ii) or (ii) to (i)  
 $b_1$  : Changing the value of first digit ( $H_1$  in (i) and  $M_1$  in (ii))  
 $b_2$  : Altering second digit ( $H_2$  in (i) and  $M_2$  in (ii))  
 $b_3$  : Altering third digit ( $M_1$  in (i) and  $S_1$  in (ii))  
 $b_4$  : Altering fourth digit ( $M_2$  in (ii) and  $S_2$  in (ii))

- We keep signals for all six digits and depending on the current mode, we use four of these six digits to be displayed.

- Timing Considerations

Assuming that the master clock has frequency 10MHz, we derive the following clocks using it.


i) ENTITY DgtCKEN

which takes 10MHz clock as input and outputs 1 at regular intervals of 1 second.

To accomplish this, we maintain a counter which goes upto  $10 \times 10^6$ , then outputs 1 indicating indicating that 1 second has been passed and then resets to 0.


ii) Refresh clock: Discussed next  $\Rightarrow$

ENTITY TODISPLAYEN

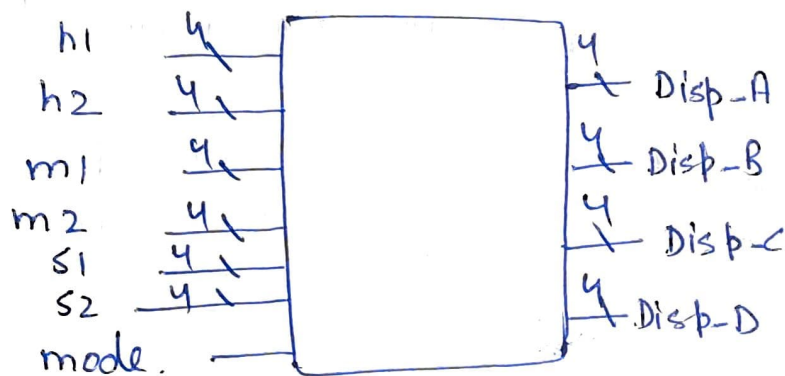

Selects which 4 digits ( $h_1, h_2, m_1, m_2$  or  $m_1, m_2, s_1, s_2$ ) are to be displayed depending whether  $mode=1$  or  $mode=0$  respectively.


P)  
ENTITY  
DgtCKEN

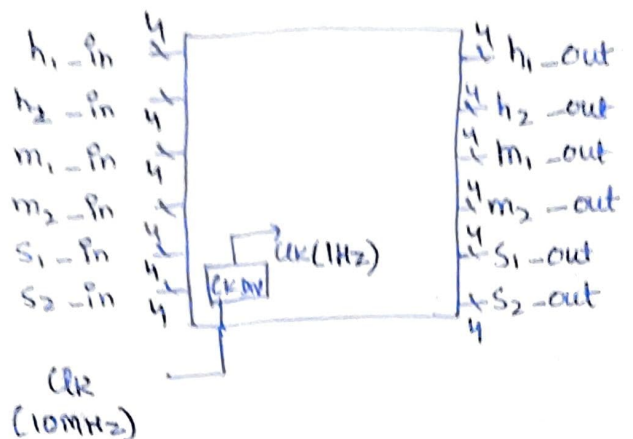

used to increment the values of  $h_1, h_2, m_1, m_2, S_1, S_2$  at regular intervals of 1 second.

We used the component CKDIVEN to reduce down the frequency from 10MHz to 1Hz.

ii) DeMUXEN

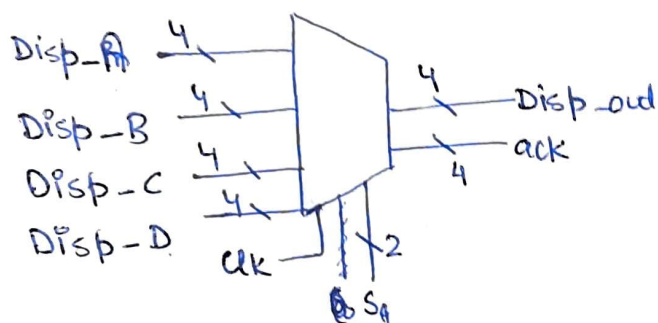

Note:  $clk(1Hz)$  and  $S$  (2 bit Vector) are output from  $ck\_clk\_div\_refreshEN$  discussed next.

The clock inputted in this circuit has refresh period of approximately 3.26 seconds.

This part of the circuit is used to figure out which of the four display inputs are to be displayed on the final display unit, at intervals of 3.2 second.

ack is a 4 bit vector for figuring out which index out of 4 is to be displayed.

if  $S = '00'$ , Disp-out = Disp-A      ack = '1000'

$S = '01'$ ,      ——— = Disp-B      ack = '0100'

$S = '10'$ ,      Disp-C      ack = '0010'


Disp-D      ack = '0001'

8  
iii) ENTITY  $\text{clk-div-refresh}$  EN

Input is 10MHz and ~~See~~ current value of Select (Indexing, as discussed ~~from~~ back).



Output  $\Rightarrow$   $\text{clk-ref}$  (ON after refresh period else off).

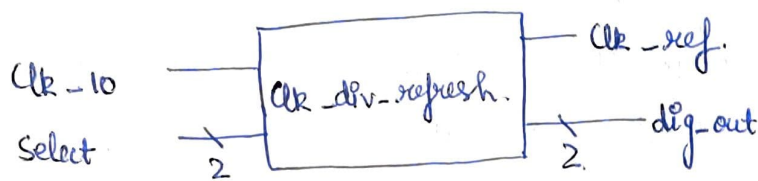$\text{dig-out} \Rightarrow$  Based on current value of select, we increment it after refresh period to indicate at what position to display next digit.



Select	$\text{dig-out}$
00	01
01	10
10	11
11	00

(iv) BCD to Seven Segment Converter.

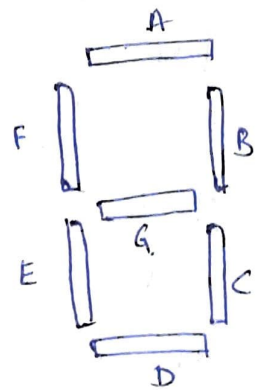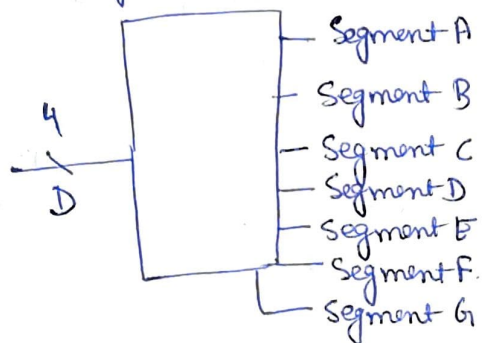

Determines which of seven segments to light up.

0000	— 111110
0001	— 0110000
0010	— 1101101
0011	— 1111001
0100	— 0110011
0101	— 1011011
0110	— 1011111
0111	— 1110000
1000	— 1111111
1001	— 1111011
else	— 0000000




## V) ENTITY Segment Display

used Components

clk-div - scfjcsdh  
Demux EN

Bcd to Seven Segment.

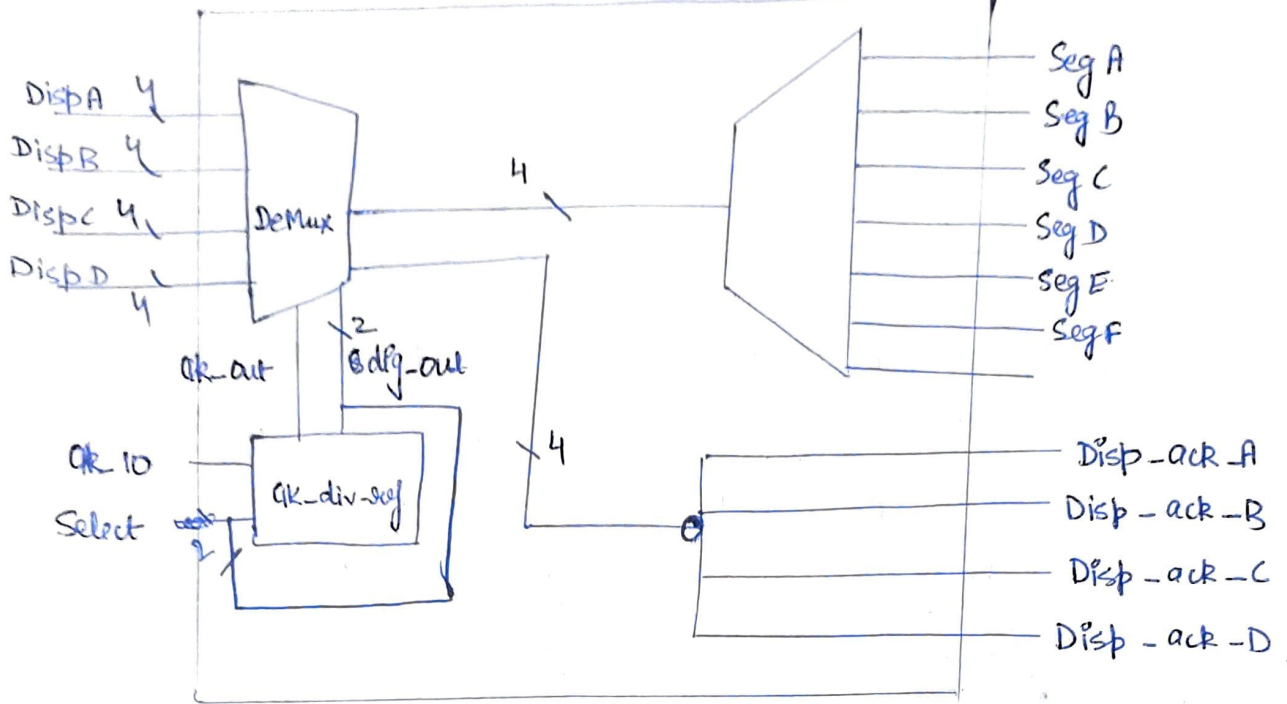

Disp-ack

0111  $\Rightarrow$  Lighting first digits and others off  
because anode is to be kept low for lighting to occur.

1011  $\Rightarrow$  second

1101  $\Rightarrow$  third

1110  $\Rightarrow$  fourth.


Note: As per the clock design, to reset the clock,  
we have to manually set all digits to 0.

# ENTITY Push Buttons

Assumption: Took the assumption that we are pressing only a single button at some instant.

Priority assigned:  $b_0 > b_1 > b_2 > b_3 > b_4$ .

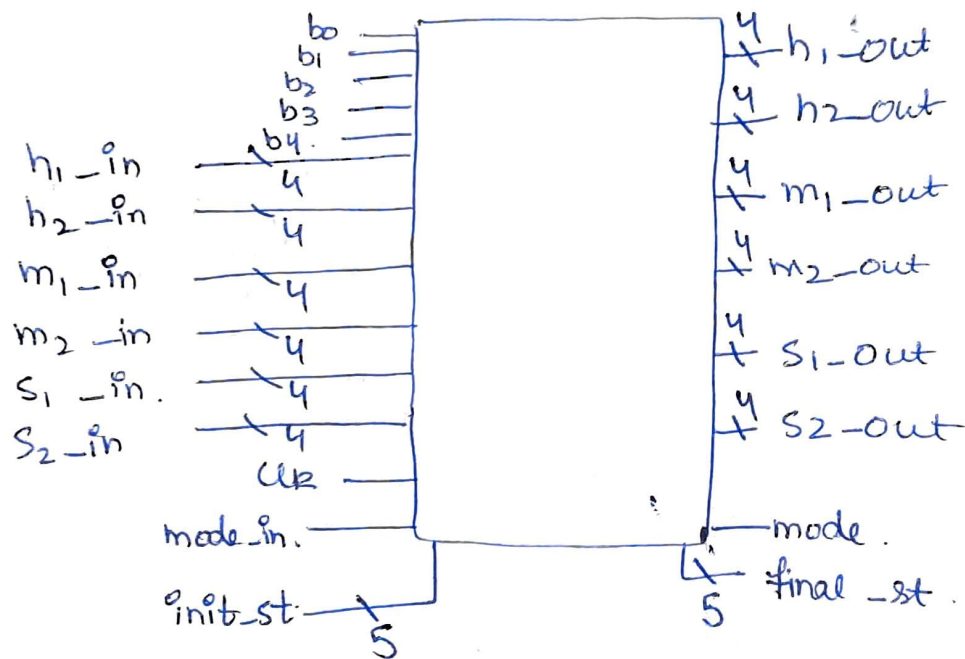We store the initial state of the clock to overcome the problem of mis-interpretation as multiple pressing since clock has time period of 100 ns and button is pressed for around some few milliseconds.



init-st is a binary vector of size 5 containing a single '1' to depict the initial state. If the value

corresponding to current button pressed in init-st is '1', we do nothing, else change the final state and perform corresponding operation.

mode: 1 (mode 1) or 0 (mode 0)

mode 1:  $h_1, h_2, m_1, m_2$

mode 0:  $m_1, m_2, s_1, s_2$

$b_0$ : change mode of display  $1 \Rightarrow 0$  or  $0 \Rightarrow 1$

$b_1$ : if mode=1, increment  $h_1$ , else increment  $m_1$

$b_2$ :  $h_2$   $m_2$

$b_3$ :  $m_1$   $s_1$

$b_4$ :  $m_2$   $s_2$

# Overall Clock Design.

